

## Chapter 2

### Test 2.1: Transmission Line Effects

For a transmission line of length  $l$  carrying a voltage wave of wavelength  $\lambda$ , phase shift and reflection effects can be ignored if:

- (a)  $l/\lambda > 1$
- (b)  $l/\lambda < 0.01$
- (c)  $l < 10$  m, regardless of the value of  $\lambda$
- (d)  $l < 1$  cm, regardless of the value of  $l$

### Test 2.2: Dispersion

A transmission line is dispersive if:

- (a) A wave is transmitted into multiple directions
- (b) A wave suffers attenuation
- (c) A rectangular pulse changes shape as it travels along the line
- (d) The velocity of a sinusoidal wave traveling on the line is independent of the wave's frequency

### Test 2.3: TEM

The acronym TEM stands for:

- (a) Transmission Eigen Mode
- (b) Transmission Elastic Mode
- (c) Transverse Elastic Mode
- (d) Transverse Electromagnetic

### Test 2.4: TEM


In a TEM mode:

- (a) The electric and magnetic fields are always orthogonal to the direction of propagation, but not to one another
- (b) At least one directional component of the electric field is orthogonal to the magnetic field
- (c) The electric and magnetic fields are parallel to one another

- (d) The electric and magnetic fields are always orthogonal to the direction of propagation, as well as to each other.
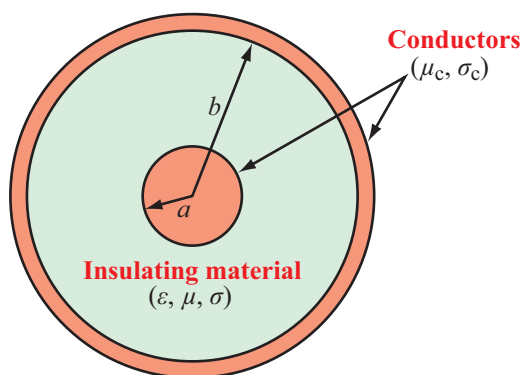
### Test 2.5: Coaxial Line


For a coaxial line with  $b = 2a$ , under what conditions is its line inductance  $L' = 0$ ?



- (a) Never
- (b)  $\epsilon = \epsilon_0$
- (c)  $\sigma_c = \infty$
- (d)  $\mu = \infty$
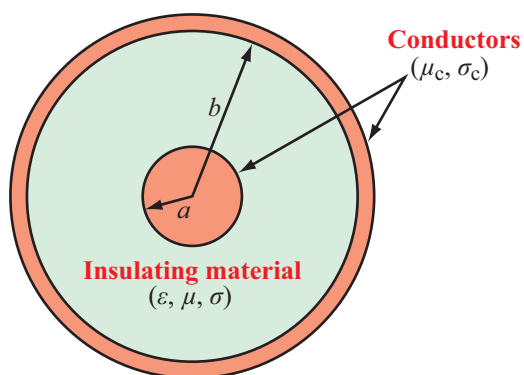
### Test 2.6: Coaxial Line

For a coaxial line with  $b = 2a$ , under what conditions is its line inductance  $G' = 0$ ?



- (a)  $\epsilon = \epsilon_0$

- (b)  $\sigma_c = \infty$
- (c)  $\mu = \infty$
- (d)  $\sigma = 0$

**Test 2.7: TEM Line**

An air-filled coaxial line with  $\epsilon = \epsilon_0$  and  $\mu = \mu_0$  has a line inductance  $L' = (1/27) \mu\text{H/m}$ . What is the line capacitance  $C'$ ?

- (a)  $C' = 0.1 \text{ nF/m}$
- (b)  $C' = 0.3 \text{ nF/m}$
- (c)  $C' = 1 \text{ nF/m}$
- (d)  $C' = 0.3 \mu\text{F/m}$

**Test 2.8: Lossless Line**

A lossless transmission line:

- (a) Is nondispersive and its  $\alpha = 0$ .
- (b) Is nondispersive but its  $\alpha$  may be  $\neq 0$ .
- (c) May or may not be dispersive, but  $\alpha = 0$ .
- (d) May or may not be dispersive and may be  $\neq 0$ .

**Test 2.9: Microstrip Line**

A  $50 \Omega$  microstrip line uses a dielectric with  $\epsilon_r = 2$ . What is the value of  $s = w/h$ ?

- (a)  $s = 4.2$
- (b)  $s = 2.1$
- (c)  $s = 0.33$
- (d)  $s = 3.33$

**Test 2.10: Reflection Coefficient**

A lossless  $50 \Omega$  line is terminated with an inductance  $L = 1 \text{ mH}$ . At  $\omega = 50 \times 10^3 \text{ rad/s}$ , what is the reflection coefficient at the end of the line?

- (a)  $\Gamma = 0$
- (b)  $\Gamma = -1$
- (c)  $\Gamma = 1e^{j\theta_r}$ , with  $\theta = -90^\circ \pm 180^\circ$
- (d)  $\Gamma = 1e^{j\theta_r}$ , with  $\theta = 45^\circ \pm 180^\circ$

**Test 2.11: SWR**

If the reflection coefficient at the load is  $|\Gamma| = 0.5e^{j30^\circ}$ , what is the SWR?

- (a)  $S = 0$
- (b)  $S = 2$
- (c)  $S = 3$
- (d)  $S = 5$

**Test 2.12: Voltage Max**

If the reflection coefficient at the load is  $|\Gamma| = 0.5e^{j30^\circ}$  and the magnitude of the incident voltage wave is  $|V_0^+| = 2$  V, what is the magnitude of the voltage maximum on the line?

- (a)  $|\tilde{V}|_{\max} = 3$  V
- (b)  $|\tilde{V}|_{\max} = 1$  V
- (c)  $|\tilde{V}|_{\max} = 4$  V
- (d)  $|\tilde{V}|_{\max} = 1.5$  V

**Test 2.13: Voltage Min**

If the reflection coefficient at the load is  $|\Gamma| = 0.5e^{j30^\circ}$  and the magnitude of the incident voltage wave is  $|V_0^+| = 2$  V, what is the magnitude of the voltage minimum on the line?

- (a)  $|\tilde{V}|_{\min} = 0$
- (b)  $|\tilde{V}|_{\min} = 0.5$  V
- (c)  $|\tilde{V}|_{\min} = 1.5$  V
- (d)  $|\tilde{V}|_{\min} = 1$  V

**Test 2.14: First Voltage Max**

If the reflection coefficient at the load is  $|\Gamma| = 0.5e^{j30^\circ}$  and  $\lambda = 60$  cm, what is the location of the voltage maximum nearest to the load?

- (a)  $d_{\max} = 1$  cm
- (b)  $d_{\max} = 2.5$  cm
- (c)  $d_{\max} = 5$  cm
- (d)  $d_{\max} = 10$  cm

**Test 2.15: First Voltage Max**

If the reflection coefficient at the load is  $|\Gamma| = 0.5e^{-j30^\circ}$  and  $\lambda = 60$  cm, what is the location of the voltage maximum nearest to the load?

- (a)  $d_{\max} = 55$  cm
- (b)  $d_{\max} = 27.5$  cm
- (c)  $d_{\max} = 18.75$  cm
- (d)  $d_{\max} = 36$  cm

**Test 2.16: Reflection Coefficient**

On a lossless transmission line, the distance between successive voltage maxima is 40 cm, the voltage maximum nearest the load is at 5 cm from the load, and  $S = 3$ . Determine  $\Gamma$ .

- (a)  $\Gamma = (0.2 + j0.1)$
- (b)  $\Gamma = (0.4 - j0.2)$
- (c)  $\Gamma = (0.35 + j0.35)$
- (d)  $\Gamma = (0.1 - j0.3)$

**Test 2.17: Equivalent Inductor**

A  $100\ \Omega$  lossless transmission line is terminated in a short circuit. The line is operated at  $f = 2$  GHz and the wavelength on the line is  $\lambda = 8$  cm. What should the length of the line be so that its input impedance is equivalent to that of an inductor with  $L_{\text{eq}} = (25/\pi)$  nH?

- (a)  $l = 1$  cm
- (b)  $l = 2$  cm
- (c)  $l = 0.5$  cm
- (d)  $l = 4$  cm

**Test 2.18: Input Impedance**

The wavelength on a  $75\ \Omega$  transmission line is 6 cm and the line length is 9 cm. If the line is terminated in  $Z_L = 150\ \Omega$ , what is the input impedance?

- (a)  $Z_{\text{in}} = 50\ \Omega$
- (b)  $Z_{\text{in}} = 75\ \Omega$
- (c)  $Z_{\text{in}} = 100\ \Omega$
- (d)  $Z_{\text{in}} = 150\ \Omega$

**Test 2.19: Input Impedance**

The wavelength on a  $75\ \Omega$  transmission line is 6 cm and the line length is 7.5 cm. If the line is terminated in  $Z_L = 150\ \Omega$ , what is the input impedance?

- (a)  $Z_{in} = 75\ \Omega$
- (b)  $Z_{in} = 37.5\ \Omega$
- (c)  $Z_{in} = 10\ \Omega$
- (d)  $Z_{in} = 150\ \Omega$


**Test 2.20: Transmitted Power**

A  $100\ \Omega$  lossless transmission line is terminated in  $Z_L = 150\ \Omega$ . What fraction of the incident average power is absorbed by the load?

- (a) Power fraction = 0.2
- (b) Power fraction = 0.4
- (c) Power fraction = 0.8
- (d) Power fraction = 0.96

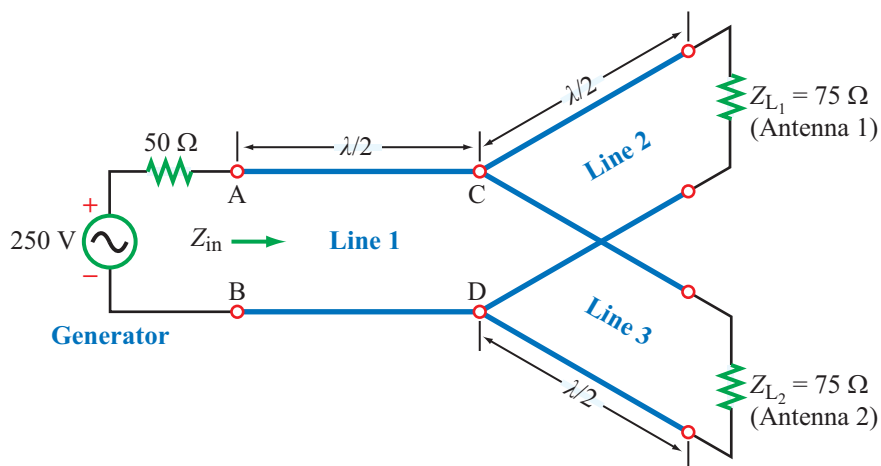**Test 2.21: Input Impedance**


For the circuit shown, what is  $Z_{in}$ ?



- (a)  $Z_{in} = 37.5\ \Omega$
- (b)  $Z_{in} = 75\ \Omega$
- (c)  $Z_{in} = 50\ \Omega$

- (d)  $Z_{\text{in}} = 100 \, \Omega$

**Test 2.22: Input Impedance**

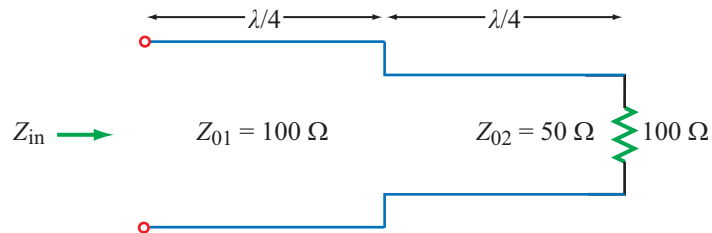

Find  $Z_{\text{in}}$ .

- (a)  $Z_{\text{in}} = 100 \, \Omega$
- (b)  $Z_{\text{in}} = 200 \, \Omega$
- (c)  $Z_{\text{in}} = 400 \, \Omega$
- (d)  $Z_{\text{in}} = 800 \, \Omega$

**Test 2.23: Impedance**

On a lossless transmission line terminated in  $Z_L = 200 \, \Omega$ , the SWR is 2.0. One possible value is  $Z_0 = 100 \, \Omega$ . What is the other possible value?

- (a)  $Z_0 = 200 \, \Omega$
- (b)  $Z_0 = 400 \, \Omega$
- (c)  $Z_0 = 50 \, \Omega$
- (d)  $Z_0 = 120 \, \Omega$

**Test 2.24: Input Impedance**

A  $25 \, \Omega$  lossless transmission line is terminated in a short circuit. Use a Smith-Chart-Module to determine the input impedance at a distance of  $0.8 \lambda$  from the load.

- (a)  $Z_{\text{in}} = 100 \, \Omega$
- (b)  $Z_{\text{in}} = j100 \, \Omega$
- (c)  $Z_{\text{in}} = -j77 \, \Omega$
- (d)  $Z_{\text{in}} = -j150 \, \Omega$

**Test 2.25: Load Impedance**

A lossless  $200\ \Omega$  transmission line  $3\lambda/8$  in length is terminated in an unknown impedance. If the input impedance is  $Z_{\text{in}} = -j5\ \Omega$ , use a Smith-Chart Module to determine  $Z_L$ .

- (a)  $Z_L = j190\ \Omega$
- (b)  $Z_L = 190\ \Omega$
- (c)  $Z_L = -j190\ \Omega$
- (d)  $Z_L = j95\ \Omega$

**Test 2.26: Input Impedance**

At an operating frequency of 5 GHz, a  $50\ \Omega$  lossless coaxial line with insulating material having a relative permittivity  $\epsilon_r = 2.25$  is terminated in an antenna with impedance  $Z_L = 100\ \Omega$ . The line length is 31 cm. Determine the input impedance.

- (a)  $Z_{\text{in}} = 50\ \Omega$
- (b)  $Z_{\text{in}} = 75\ \Omega$
- (c)  $Z_{\text{in}} = 25\ \Omega$
- (d)  $Z_{\text{in}} = 100\ \Omega$

**Test 2.27: Quarter-Wave Transformer**

A lossless  $25\ \Omega$  line is terminated in a load impedance  $Z_L = (50 - j100)\ \Omega$ . To eliminate reflections, a quarter-wave transformer with impedance  $Z_{02} = 7.75\ \Omega$  is inserted at a distance  $d$  from the load. If  $\lambda = 30\ \text{cm}$ , what is the value of  $d$ ?

- (a)  $d = 10\ \text{cm}$
- (b)  $d = 6.5\ \text{cm}$
- (c)  $d = 13\ \text{cm}$
- (d)  $d = 1.5\ \text{cm}$

**Test 2.28: Quarter-Wave Transformer**

A lossless  $25\ \Omega$  line is terminated in a load impedance  $Z_L = (50 - j100)\ \Omega$ . To eliminate reflections, a quarter-wave transformer was inserted at a distance of 6.5 cm from the load. If  $\lambda = 30\ \text{cm}$ , what is the characteristic impedance of the quarter-wave transformer?


- (a)  $Z_{02} = 7.75\ \Omega$
- (b)  $Z_{02} = 25\ \Omega$



- (c)  $Z_{02} = 50 \, \Omega$
- (d)  $Z_{02} = 100 \, \Omega$

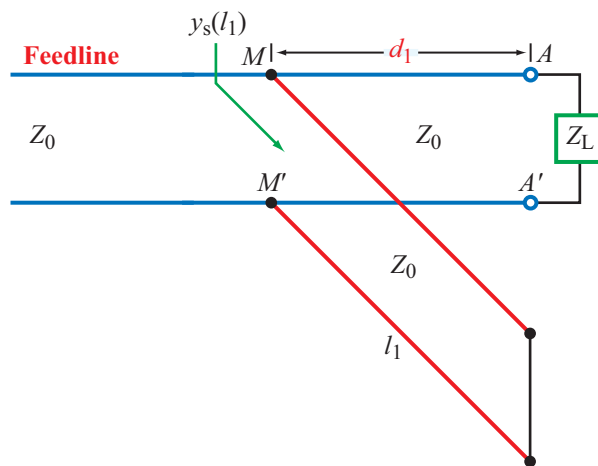**Test 2.29: Matching**

A  $100 \, \Omega$  lossless line is to be matched to an antenna with  $Z_L = (150 - j40) \, \Omega$  using a shorted stub. For perfect matching, it was determined that the stub should be inserted at  $d_1 = 0.104\lambda$  from the load. What should the length of the stub  $l_1$  be?



- (a)  $l_1 = 0.25\lambda$
- (b)  $l_1 = 0.35\lambda$
- (c)  $l_1 = 0.5\lambda$
- (d)  $l_1 = 0.17\lambda$


**Test 2.30: Matching**

A  $100 \, \Omega$  lossless line is to be matched to an antenna with  $Z_L = (150 - j40) \, \Omega$  using a shorted stub. For perfect matching, it was determined that the stub should be inserted at  $d_1$  from the load and its length should be  $l_1 = 0.173\lambda$ . What is the value of  $d_1$ ?

- (a)  $d_1 = 0.3\lambda$
- (b)  $d_1 = 0.2\lambda$
- (c)  $d_1 = 0.1\lambda$
- (d)  $d_1 = 0.05\lambda$

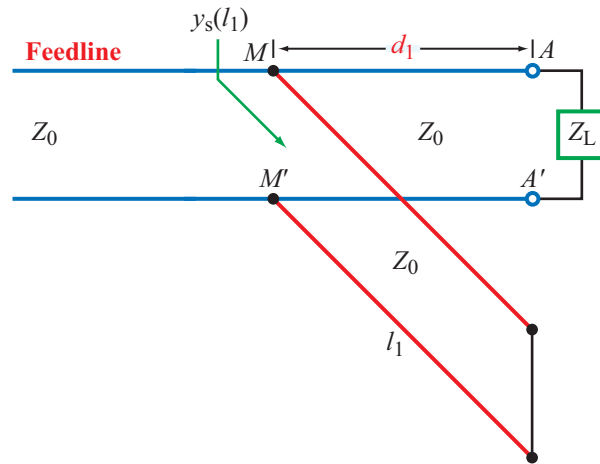**Test 2.31: Impedance Matching**

A  $100\ \Omega$  lossless line is to be matched to an antenna with  $Z_L = (200 + j100)\ \Omega$  using a shorted stub. For perfect matching, it was determined that the stub should be inserted at  $d_1 = 0.2\lambda$  from the load. What should the length of the stub  $l_1$  be?



- (a)  $l_1 = 0.125\lambda$
- (b)  $l_1 = 0.25\lambda$
- (c)  $l_1 = 0.375\lambda$
- (d)  $l_1 = 0.5\lambda$


### Test 2.32: Impedance Matching

A  $100\ \Omega$  lossless line is to be matched to an antenna with  $Z_L = (200 + j100)\ \Omega$  using a shorted stub. For perfect matching, it was determined that the stub should be inserted at  $d_1$  from the load and its length should be  $l_1 = 0.125\lambda$ . What is the value of  $d_1$ ?

- (a)  $d_1 = 0.1\lambda$
- (b)  $d_1 = 0.2\lambda$
- (c)  $d_1 = 0.3\lambda$
- (d)  $d_1 = 0.4\lambda$
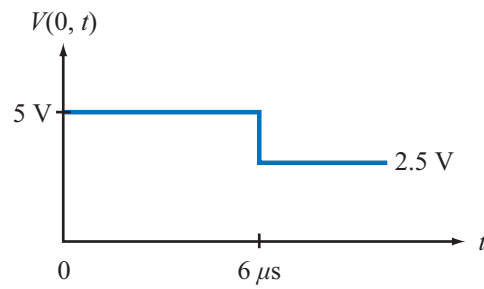
### Test 2.33: Transient Response


In response to a step voltage, the voltage waveform shown in the figure was observed at the sending end of a lossless transmission line with  $R_g = Z_0 = 150\ \Omega$  and  $\epsilon_r = 9$ . Determine the length of the line.



- (a)  $l = 150 \text{ m}$
- (b)  $l = 300 \text{ m}$
- (c)  $l = 450 \text{ m}$
- (d)  $l = 600 \text{ m}$
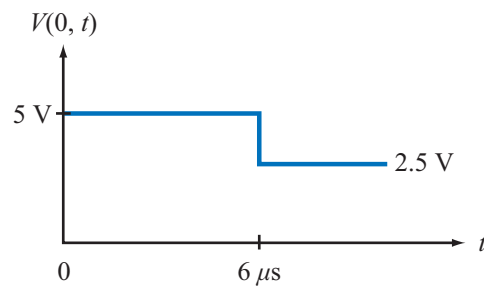
### Test 2.34: Transient Response

In response to a step voltage, the voltage waveform shown in the figure was observed at the sending end of a lossless transmission line with  $R_g = Z_0 = 150 \Omega$  and  $\epsilon_r = 9$ . Determine the load impedance.



- (a)  $Z_L = 25 \Omega$
- (b)  $Z_L = 100 \Omega$
- (c)  $Z_L = 150 \Omega$
- (d)  $Z_L = 50 \Omega$